



# FFE EQUALIZER

## Digital Design (ELC4007)

Names	ID
ابانوب عطية سعيد	9202026
أحمد ابراهيم محمد عبد المعطى	9202045
محمد محسن كمال موسى	9203326
محمود شريف محمود حسن	9203409
فاطمة عادل شعبان	9203047
بسمه وليد حسنى ابوهاشم عشرى	9202383

Submitted to: Dr. Karem Osama, Eng. Mahmoud Yehia.

# Introduction


A Feed-Forward Equalizer (FFE) is essential in high-speed digital communication for combating inter-symbol interference (ISI), which distorts signals during transmission. By applying adjustable coefficients to the incoming signal, an FFE reshapes it to counteract distortions, improving signal integrity and enabling higher data rates.

Key aspects of FFE include:

- **Taps and Coefficients:** Adjustable weights applied to signal samples to minimize ISI.
- **Adaptive Algorithms:** Real-time adjustment of coefficients using algorithms like LMS and RLS.
- **Performance Metrics:** Measured by improvements in bit error rate (BER) and signal-to-noise ratio (SNR).


FFEs are crucial in standards like Ethernet, USB, PCIe, and optical fiber communications, ensuring reliable and efficient data transmission over challenging channels.

## Hardware Design of FEE

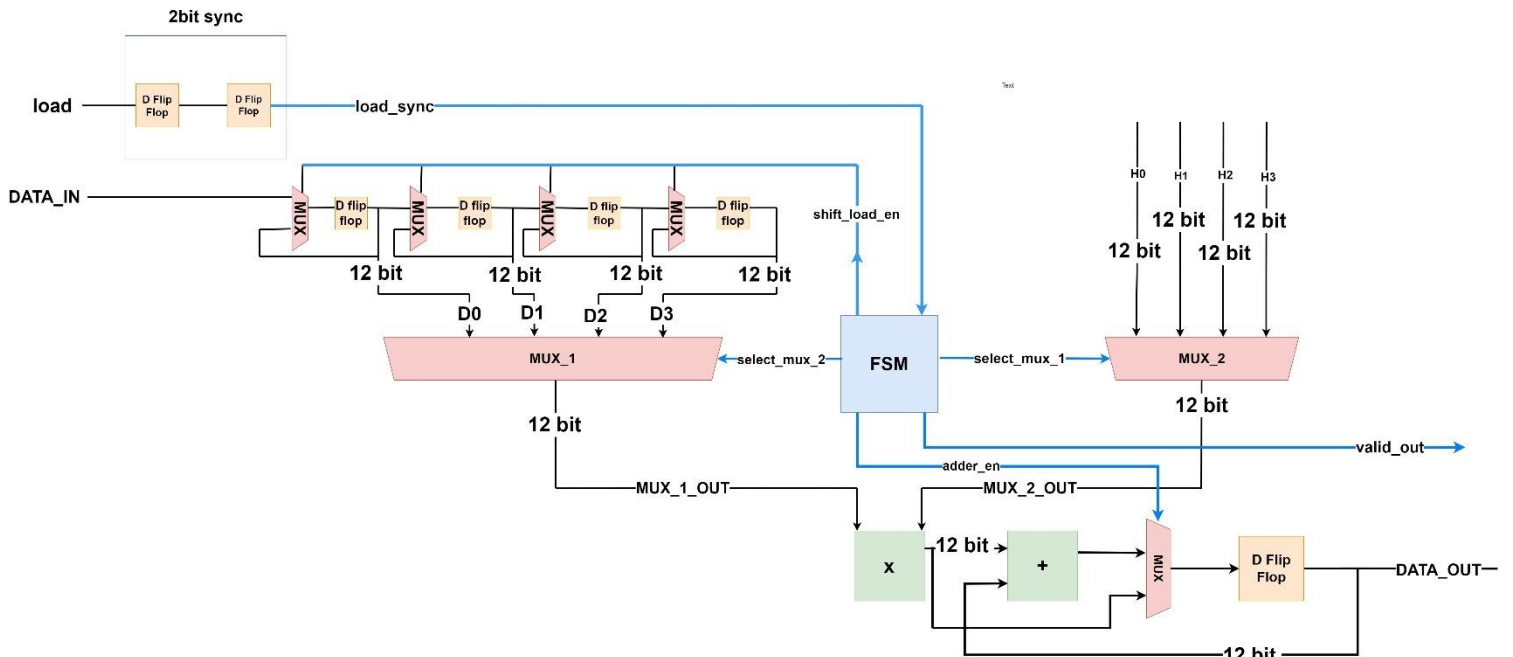


## Sub-Blocks Description

### ➤ Shift Register:

 


Port	Direction	Width	Description	Connected to
DATA_IN	IN	12	Input data comes from TX	Top input port
Shift_load_en	IN	1	Control signal to enable shift operation	FSM
D0	OUT	12	Registered Values	MUX_1
D1	OUT	12	Registered Values	MUX_1
D2	OUT	12	Registered Values	MUX_1
D3	OUT	12	Registered Values	MUX_1

### ➤ Two-bit synchronizer

 

Port	Direction	Width	Description	Connected to
Load	IN	1	Input signal comes from TX	Top input port
Load_sync	OUT	1	Synchronize version of Load signal	FSM

- **Multiplier:** We use a 12-bit multiplier that will multiply at each clock cycle of the FFE one of the data words by one of the FFE tabs. After doing Fixed Point Analysis, we chose to divide those 12-bit operands to 6-bits for the integer part and 6-bits for fractions. The output would be 24-bits, and we will take only 12-bits from bit (6) to bit (17) to represent the output, 6-bits of them from bit(6) to bit(11) represent the fractional part, and the rest from bit(12) to bit(17) represent the integer part of the output.
- **Adder:** We have a 12-bit adder, the output each time would be 13-bits, but we truncate the Least Significant Bit. After receiving the load signal, the adder starts by adding the multiplier output to 0 in the first clock cycle and in the next cycles it begins accumulating the multiplier outputs to each other.
- **FSM:**

 

- **Note:**
  - For each Flip Flop there is port for **clock** and port for **Reset**
  - The **clock** of all Flip Flop is the FFE clock frequency (4 MHz)
  - All internal signals are signed signal with 12 bit width
  - **adder\_en** signal decided if Register on output port will store output of Adder or output of Multiplier

# Pseudo Code

---

**ALGORITHM 1 : ALGORITHM TO PERFORM FFE EQUATION  $y_i = \sum_{j=0}^{j=3} h_j D_{i-j}$**

---

```
1  INPUT DATA_IN : Data come from TX
2  INPUT load : Signal come from TX to ensure the validity of the data
3  INPUT clk : clock signal
4  INPUT rst : reset signal
5  OUTPUT DATA_OUT : Result from FIR
6  INITIALIZE : D0 ,D1 ,D2 ,D3 , valid_out and DATA_OUT to zero

7  AT every positive edge of clk
8      IF rst is active low THEN
9          SET current_state = S0
10     ELSE
11         SET next_state to current_state
12     ENDIF
13 ENDAT

14 SWITCH current_state
15     CASE S0 :
16         IF load is low THEN
17             SET next_state = S0
18         ELSE
19             SET next_state = S1
20             SET shift_load_en = 1
21         ENDIF
22     CASE S1 :
23         CALCULATE DATA_OUT = D0 * H0 + 12'b0
24         SET next_state = S2
25     CASE S2 :
26         CALCULATE DATA_OUT = D1*H1 + D0 * H0
27         SET next_state = S3
28     CASE S3 :
29         CALCULATE DATA_OUT = D2*H2 + D1*H1 + D0 * H0
30         SET next_state = S4
31     CASE S4 :
32         CALCULATE DATA_OUT = D3*H3 + D2*H2 + D1*H1 + D0 * H0
33         IF load is low THEN
34             SET next_state = S0
35         ELSE
36             SET next_state = S1
37             SET shift_load_en = 1
38 ENDSWITCH
```

## Pseudo Code (More Details)

```
//_____Top System _____:
inputs: load,Data_in[12],CLK,RST

outputs:Data_out[12] ,valid_output


// values for filter taps
h0=12'b 000000100000
h1=12'b 111111110000
h2=12'b 000000001010
h3=12'b 111111111100


//***** BIT_SYNCHONIZER*****

    input    CLK
    input    RST
    input    load
    output   load_sync

//LOGIC design:
internal flipflop reg_sync[2]

every +ve CLK or -ve RST

    if(!RST)
    {
        reg_sync=0
    }

else
{
    reg_sync[0]=reg_sync[1]
    reg_sync[1] = load
}
```

we make this connection :

```
load_sync = reg_sync[0]
```

```
//*****shift_reg *****
```

```
input          CLK
input          RST
input          shift_load_en
input          Data_in
output         shift_reg_out[48]
```

```
//LOGIC design:
```

```
every +ve CLK or -ve RST {
```

```
if (!RST)
```

```
{
    shift_reg_out = 0
}
```

```
else if (shift_load_en){
```

```
    //SHIFT RIGHT & CAPTURE Inputs
```

```
    shift_reg_out[11:0] = shift_reg_out[23:12]
```

```
    shift_reg_out[23:12] = shift_reg_out[24:35]
```

```
    shift_reg_out[24:35] = shift_reg_out[47:36]
```

```
    shift_reg_out[47:36] = Data_in
```

```
}
```

```
else
```

```
    // retain old value
```

```
    shift_reg_out = shift_reg_out
```

```
}
```

```
//*****MUX1*****:
```

```
inputs: h0,h1,h2,h3,select_mux_1
```

```
output:h_i[12]
```

```

//LOGIC design:
case(select_mux_2)
0: h_i= h0
1: h_i= h1
2: h_i= h2
3: h_i= h3

//*****MUX2*****:
inputs: shift_reg_out[11:0],shift_reg_out[23:12],
shift_reg_out[24:35],shift_reg_out[47:36],select_mux_2

output: D_i[12]

//LOGIC design:
case(select_mux_2)
0: D_i= shift_reg_out[11:0]
1: D_i= shift_reg_out[23:12]
2: D_i= shift_reg_out[24:35]
3: D_i= shift_reg_out[47:36]

//***** multilplier block *****
    input    D_i,h_i
    output   mul_out[24]

    //LOGIC design:
    while(1){
        mul_out = D_i*h_i
    }

//***** adder_block*****

    input    CLK
    input    RST
    input    adder_en
    input    mul_out[11:0],Data_out_ff    // we trim MSB from

```



```

multilplier output
    output    Data_out

//LOGIC design:
every +ve CLK edge or -ve RST edge {
    if(!RST)
        Data_out=0
    else
    {
        if(adder_en)
        {
            Data_out = mul_out + [11:0],Data_out_ff
        }
        else
        {
            Data_out=mul_out
        }

    }

}

//*****Finite State Machine*****//
input    CLK
input    RST
input    load_sync
output   adder_en,valid_output
output   select_mux_1
output   select_mux_2
output   shift_load_en

//we start at initial state s0 (current_state = s0) until
Load_Sig is asserted

//every clock edge we make current_state = next_state

// also we go to s0 on a -ve edge reset

```

```

case(current_state)
s0:
// ctrl signals :
adder_en          = 0
select_mux_1      = 0
select_mux_2      = 0
valid_output = 0

if(load_sync == 1) {
next_state        = s1
shift_load_en     = 1
}
else{
next_state        = s0
shift_load_en     = 0
}


s1:
// ctrl signals :
select_mux_1      = 0
select_mux_2      = 0
shift_load_en     = 0
valid_output = 0


next_state        = s2


s2:
// ctrl signals:

select_mux_1      = 1
select_mux_2      = 1
shift_load_en     = 0
valid_output = 0


next_state        = s3


s3:

```

```
// ctrl signals:
select_mux_1      = 2
select_mux_2      = 2
shift_load_en     = 0
valid_output      = 0

next_state        = s4

s4:
// ctrl signals :
select_mux_1      = 3
select_mux_2      = 3
valid_output      = 1

if(load == 1){
    next_state = s1
    shift_load_en = 1
} else {
    Next_state = s0
    Shift_load_en = 0
}
```


# Verilog Simulation

```
# input data : 15
# output is 7.500000
# result should be 7.500000
#
# -----
#
# input data : 20
# output is 6.250000
# result should be 6.250000
#
# -----
#
# input data : 29
# output is 11.843750
# result should be 11.843750
#
# -----
#
# input data : 30
# output is 9.937500
# result should be 9.937500
#
# -----
#
# input data is -16.500000
# output is -12.468750
# result should be -12.468750
```

- $y_i = -12.468750$

by apply equation  $y_i = \sum_{j=0}^{j=3} h_j D_{i-j}$  :

- **For first input (15):**
  - $y_i = 15 * h_0 = 15 * 0.5 = 7.5$
- **For second input (20) :**
  - $y_i = 20 * h_0 + 15 * h_1$
  - $y_i = 20 * 0.5 - 15 * 0.25 = 6.25$
- **For third input (29) :**
  - $y_i = 29 * h_0 + 20 * h_1 + 15 * h_2$
  - $y_i = 29 * 0.5 - 20 * 0.25 + 15 * 0.15625$
  - $y_i = 11.84375$
- **For fourth input (30) :**
  - $y_i = 30 * h_0 + 29 * h_1 + 20 * h_2 + 15 * h_3$
  - $y_i = 30 * 0.5 - 29 * 0.25 + 20 * 0.15625 - 15 * 0.0625$
  - $y_i = 9.9375$
- **For fifth input (-16) :**
  - $y_i = -16 * h_0 + 30 * h_1 + 29 * h_2 + 20 * h_3$
  - $y_i = -16 * 0.5 - 30 * 0.25 + 29 * 0.15625 - 20 * 0.0625$

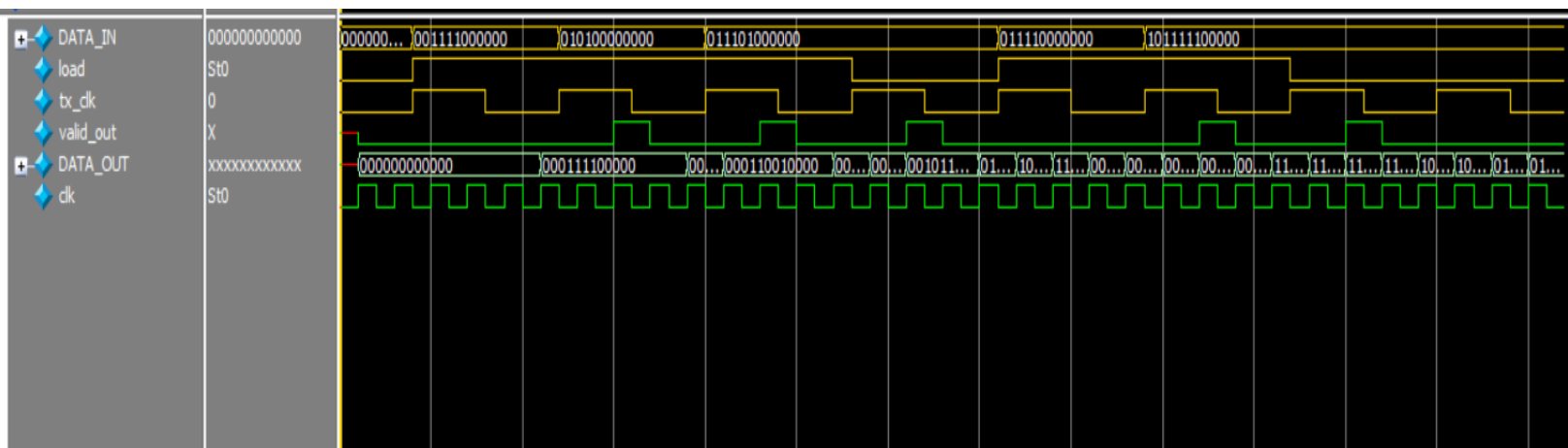

## Synthesis:

